

CSE 4207 CT 4 Assignment

Roll No: 1903048

Assignment Problem:

Category: A

Word Size = 7bits

ALU Operations = NOT ,ROR

HDL Code:

Check List: Have you added all the modules written in verilog including ALU, ALU_OP1, ALU_OP2, ALU_TESTBENCH?	YES
--	-----

ALU_OP1.v

```
module ALU_OP1
(
    input wire [6:0] A,
    output wire [6:0] R
);
    assign R = ~A;
endmodule
```

ALU_OP2.v

```
module ALU_OP2
(
    input wire [6:0] A,
    input wire [2:0] B,          // Number of bits to rotate (0-
7)
    output reg [6:0] R
);
    always @(*) begin
        case (B)
            3'd0: R = A;
// No rotation
            3'd1: R = {A[0], A[6:1]};
            3'd2: R = {A[1:0], A[6:2]};
            3'd3: R = {A[2:0], A[6:3]};
            3'd4: R = {A[3:0], A[6:4]};
            3'd5: R = {A[4:0], A[6:5]};
            3'd6: R = {A[5:0], A[6]};
            3'd7: R = A; // Full rotate results in original
            default: R = A;
        endcase
    end
endmodule
```

ALU.v

```
module ALU
(
    input wire [6:0] A, B,
    input wire [1:0] OP,          // 00 = NOT, 01 = ROR
    output reg [6:0] R,
    output wire CF,
    output wire SF,
    output wire ZF
);

    wire [6:0] R_NOT, R_ROR;

    // Submodules
    ALU_OP1 NOT1 (.A(A), .R(R_NOT));
    ALU_OP2 ROR1 (.A(A), .B(B[2:0]), .R(R_ROR));

    always @(*) begin
        case (OP)
            2'b00: R = R_NOT;
            2'b01: R = R_ROR;
            default: R = 7'b0000000;
        endcase
    end

    assign CF = (OP == 2'b01) ? A[B % 7] : 1'b0; // CF is
last bit rotated out
    assign SF = R[6];                          // Sign flag
(MSB)
    assign ZF = ~(|R);                          // Zero flag
endmodule
```

ALU_TESTBENCH.v

```
module ALU_TESTBENCH;
    reg [6:0] A, B;
    reg [1:0] OP;
    wire [6:0] R;
    wire CF, SF, ZF;

    ALU uut (
        .A(A),
        .B(B),
        .OP(OP),
        .R(R),
        .CF(CF),
        .SF(SF),
        .ZF(ZF)
    );
endmodule
```

```

);

initial begin
    $dumpfile("test7.vcd");
    $dumpvars(0, ALU_TESTBENCH);

    // Test NOT operation
    A = 7'b1010101; B = 7'b0000000; OP = 2'b00; #10;
    A = 7'b0000000; B = 7'b0000000; OP = 2'b00; #10;

    // Test Rotate Right by various amounts
    A = 7'b1000001; B = 7'b0000001; OP = 2'b01; #10; //
Rotate by 1
    A = 7'b1100001; B = 7'b0000010; OP = 2'b01; #10; //
Rotate by 2
    A = 7'b1111111; B = 7'b0000101; OP = 2'b01; #10; //
Rotate by 5
    A = 7'b1000000; B = 7'b0000011; OP = 2'b01; #10; //
Rotate by 3
    A = 7'b0000001; B = 7'b0000011; OP = 2'b01; #10; //
Rotate by 3
    A = 7'b1000001; B = 7'b0000000; OP = 2'b01; #10; //
Rotate by 0
    A = 7'b1000001; B = 7'b0000111; OP = 2'b01; #10; //
Rotate by 7 (same as original)


    $finish;
end

initial begin
    $monitor("Time=%0t A=%b B=%b OP=%b -> R=%b CF=%b
ZF=%b SF=%b", $time, A, B, OP, R, CF, ZF, SF);
end
endmodule

```

RTL Timing Diagram:

Check List: Have you added all the timing diagrams of ALU_TESTBENCH?	YES
---	-----

 

Category: B

Word Size = 7bits

ALU Operations = NOT ,ROR

RTL Synthesis (130nm Skywater PDK with OpenLane toolchain):

Check List: Have you added <i>RTL synthesis summary</i> , <i>RTL synthesized design figure</i> and <i>Standard cell usage in synthesized design</i> ?	YES
--	-----

RTL synthesis summary

=== ALU ===


METRIC	COUNT
Number of wires:	134
Number of wire bits:	153
Number of public wires:	7
Number of public wire bits:	26
Number of ports:	7
Number of port bits:	26
Number of memories:	0
Number of memory bits:	0
Number of processes:	0
Number of cells:	137

Standard cell usage in synthesized design

sky130_fd_sc_hd__a2111oi_2	1
sky130_fd_sc_hd__a211o_2	4
sky130_fd_sc_hd__a21bo_2	2
sky130_fd_sc_hd__a21o_2	5
sky130_fd_sc_hd__a21oi_2	4
sky130_fd_sc_hd__a221o_2	3
sky130_fd_sc_hd__a221oi_2	3
sky130_fd_sc_hd__a22o_2	1
sky130_fd_sc_hd__a311o_2	1
sky130_fd_sc_hd__a31o_2	4
sky130_fd_sc_hd__a31oi_2	1
sky130_fd_sc_hd__a32o_2	2
sky130_fd_sc_hd__and2_2	4
sky130_fd_sc_hd__and2_4	1
sky130_fd_sc_hd__and3_2	4
sky130_fd_sc_hd__and4b_2	1
sky130_fd_sc_hd__buf_2	1
sky130_fd_sc_hd__inv_2	12
sky130_fd_sc_hd__mux2_1	3

sky130_fd_sc_hd__mux2_2	4
sky130_fd_sc_hd__mux4_2	8
sky130_fd_sc_hd__nand2_2	9
sky130_fd_sc_hd__nand2b_2	2
sky130_fd_sc_hd__nand3_2	2
sky130_fd_sc_hd__nand3b_2	1
sky130_fd_sc_hd__nor2_2	7
sky130_fd_sc_hd__nor2b_2	1
sky130_fd_sc_hd__nor3_2	1
sky130_fd_sc_hd__nor3b_2	1
sky130_fd_sc_hd__nor4_4	1
sky130_fd_sc_hd__nor4b_2	1
sky130_fd_sc_hd__o211a_2	8
sky130_fd_sc_hd__o211a_4	2
sky130_fd_sc_hd__o211ai_2	1
sky130_fd_sc_hd__o21a_2	5
sky130_fd_sc_hd__o21bai_2	1
sky130_fd_sc_hd__o22a_2	1
sky130_fd_sc_hd__o2bb2a_2	1
sky130_fd_sc_hd__o311a_2	1
sky130_fd_sc_hd__o31a_2	3
sky130_fd_sc_hd__o31ai_2	1
sky130_fd_sc_hd__o32ai_2	1
sky130_fd_sc_hd__or2_2	6
sky130_fd_sc_hd__or2_4	2
sky130_fd_sc_hd__or3_2	1
sky130_fd_sc_hd__or3_4	2
sky130_fd_sc_hd__or3b_2	1
sky130_fd_sc_hd__or4_4	1
sky130_fd_sc_hd__xnor2_2	2
sky130_fd_sc_hd__xor2_2	2

RTL synthesized design figure

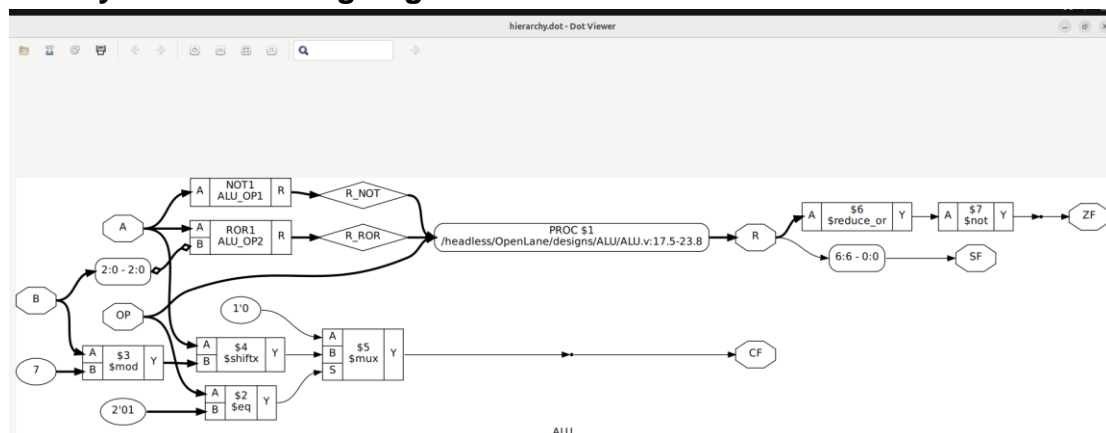

RTL Floorplan (130nm Skywater PDK with OpenLane toolchain)


```
33 [INFO] Extracting DIE_AREA and CORE_AREA from the floorplan
34 [INFO] Floorplanned on a die area of 0.0 0.0 150.0 150.0 (µm).
35 [INFO] Floorplanned on a core area of 5.52 10.88 144.44 138.72 (µm).
36 Writing metric design__die__bbox: 0.0 0.0 150.0 150.0
37 Writing metric design__core__bbox: 5.52 10.88 144.44 138.72
38 Setting global connections for newly added cells...
39 [INFO] Setting global connections...
40 Updating metrics...
41 Cell type report:
42   Buffer                      Count      Area
43   Inverter                   12         45.04
44   Multi-Input combinational cell 124       1323.77
45   Total                      137       1373.82
```

RTL Power Analysis (130nm Skywater PDK with OpenLane toolchain)


Open [icon] power.rpt
~/OpenLane/designs/ALL/runs/RUN_2025-06-08_07-50-03/54-openroad-stapostpnr/nom_tt_025C_1v80

1
2 =====
3 report_power
4 =====
5 ===== nom_tt_025C_1v80 Corner =====
6
7 Group Internal Switching Leakage Total
8 Power Power Power Power (Watts)
9 -----
10 Sequential 0.000000e+00 0.000000e+00 0.000000e+00 0.000000e+00 0.0%
11 Combinational 1.324999e-05 1.740464e-05 7.347346e-10 3.065537e-05 100.0%
12 Clock 0.000000e+00 0.000000e+00 1.240943e-09 1.240943e-09 0.0%
13 Macro 0.000000e+00 0.000000e+00 0.000000e+00 0.000000e+00 0.0%
14 Pad 0.000000e+00 0.000000e+00 0.000000e+00 0.000000e+00 0.0%
15 -----
16 Total 1.324999e-05 1.740464e-05 1.975678e-09 3.065661e-05 100.0%
17 43.2% 56.8% 0.0%
18 |

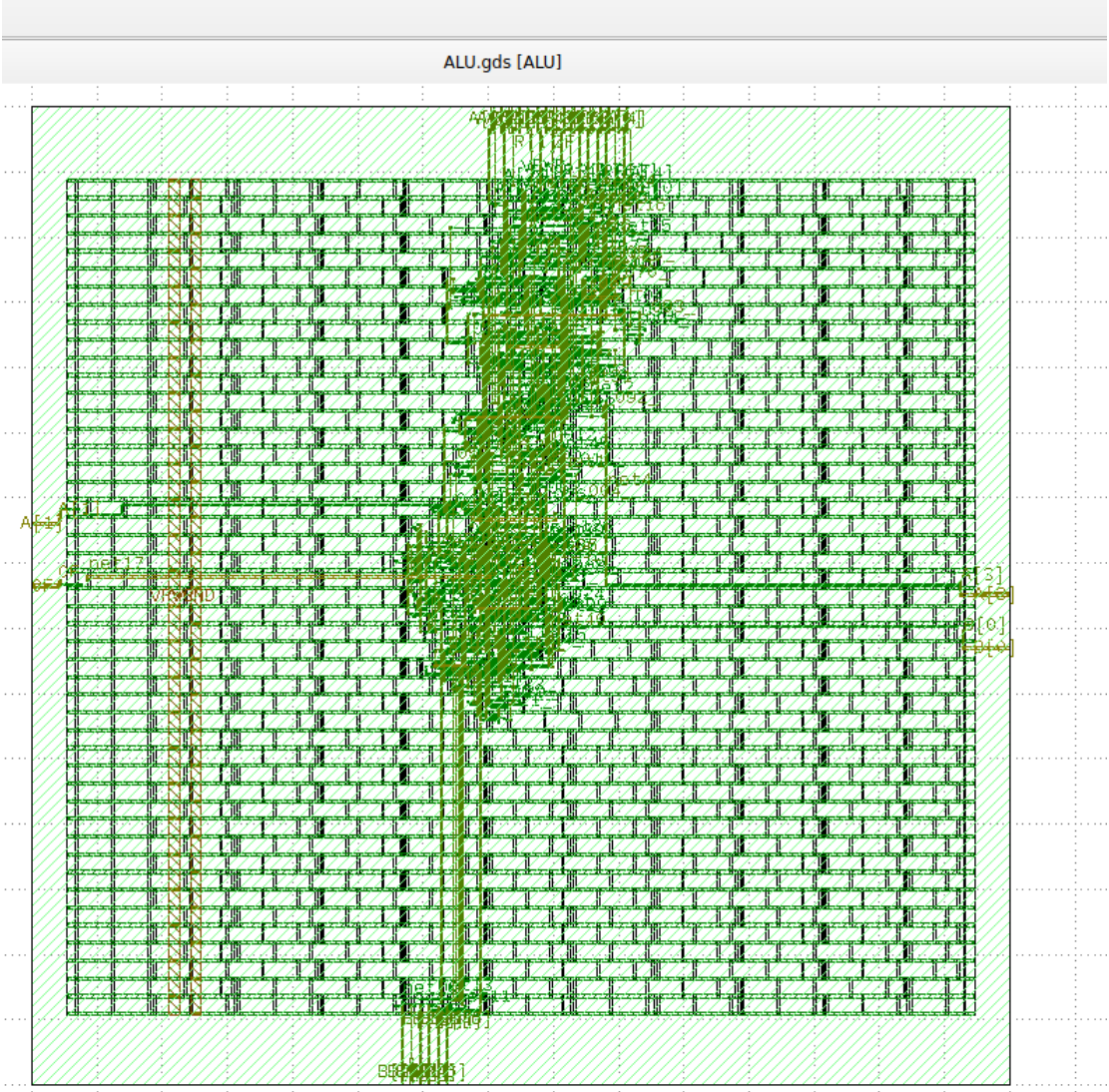GDS Layout (130nm Skywater PDK with OpenLane toolchain)



 Heatmap (130nm Skywater PDK with OpenLane toolchain)



Category: C

Word Size = 7bits

ALU Operations = NOT ,ROR

HDL Code:

Check List: Have you added all the modules written in verilog including CONTROLLER,TOP, TOP_TESTBENCH,CONTROLLER_TESTBENCH?	YES
--	-----

TOP.v

```
module TOP(  
    input wire clk, reset,  
    output wire [6:0] result,  
    output wire flag  
);  
  
wire [6:0] a, b;  
wire [2:0] op;  
wire [6:0] res;  
wire f;
```



```

CONTROLLER controller(
    .clk(clk), .reset(reset),
    .a(a), .b(b), .op(op),
    .result(res),
    .flag(f)
);

CONTROLLER_TESTBENCH datapath(
    .a(a), .b(b), .op(op),
    .result(res), .flag(f)
);

assign result = res;
assign flag = f;

endmodule

```

TOP_CONTROLLER.v

```

`timescale 1ns/1ns

module TOP_TESTBENCH;
    reg clk, reset;
    wire [6:0] result;
    wire flag;

    TOP top (
        .clk(clk), .reset(reset),
        .result(result), .flag(flag)
    );

    initial begin
        clk = 0;
        forever #5 clk = ~clk;
    end

    initial begin
        $dumpfile("alu_fsm.vcd");
        $dumpvars(0, TOP_TESTBENCH);

        reset = 1;
        #10;
        reset = 0;

        #100; // Run for a few clock cycles
        $finish;
    end
endmodule

```

CONTROLLER.v

```
module CONTROLLER(
    input wire clk, reset,
    output reg [6:0] a, b,
    output reg [2:0] op,
    input wire [6:0] result,
    input wire flag
);

reg [2:0] state, next_state;

parameter START = 3'b000,
           ONE   = 3'b001,
           TWO   = 3'b010,
           THREE = 3'b011,
           FINISH = 3'b100;

always @(posedge clk or posedge reset) begin
    if (reset) state <= START;
    else state <= next_state;
end

always @(*) begin
    a = 7'd0; b = 7'd0; op = 3'd0;
    case (state)
        START: next_state = ONE;
        ONE: begin
            a = 7'b0101010; op = 3'd0; // NOT
            next_state = TWO;
        end
        TWO: begin
            a = 7'b0001101; op = 3'd1; // ROTATE RIGHT
            next_state = THREE;
        end
        THREE: begin
            a = 7'd0; op = 3'd2;          // NOP or final test
        end
        case
            next_state = FINISH;
        end
        FINISH: next_state = FINISH;
        default: next_state = START;
    endcase
end

endmodule
```

CONTROLLER_TESTBENCH.v

```

module TOP(
    input wire clk, reset,
    output wire [6:0] result,
    output wire flag
);

wire [6:0] a, b;
wire [2:0] op;
wire [6:0] res;
wire f;

CONTROLLER controller(
    .clk(clk), .reset(reset),
    .a(a), .b(b), .op(op),
    .result(res),
    .flag(f)
);

CONTROLLER_TESTBENCH datapath(
    .a(a), .b(b), .op(op),
    .result(res), .flag(f)
);

assign result = res;
assign flag = f;

endmodule

```

RTL Timing Diagram:

Check List: Have you added all the timing diagrams of CONTROLLER_TESTBENCH, TOP_TESTBENCH?	YES
---	-----

